

Knowledge is Power...

Ivington CofE Primary and Preschool



Reaching together... stand firm in your faith, be courageous and strong - 1 Corinthians 16:13

SUBJECT: PHYSICS - ELECTRICITY	TERM: SUMMER 2022		YEAR GROUPS 4/5		
What should I already know?		Vocabulary			
 Electricity is a form of energy that can be carried by wires and is used for heating and lighting, and to provide power for devices. Sources of light and sound may need electricity to work. 	appliances	a device or machine in your home that you use to do a job such as cleaning or cooking. Appliances are often electrical.	energy	the power from sources such as electricity that makes machines work or provides heat	
	battery	small devices that provide the power for	fuel	a substance such as coal, oil, or petrol that is burned to provide heat or power	
What will I know by the end of the unit?	bulb	the glass part of an electric lamp, which gives out light when electricity passes	Generate	cause it to begin and develop	
 Where does electricity come from? Electricity is generated using energy from natural sources such as the Sun, oil, waterand wind. These can also be called fuel sources. 	buzzer	through it. an electrical device that is used to make a buzzing sound	Insulator	a non-conductor of electricity or heat	
	cell	a synonym for battery	Mains	where the supply of water, electricity , or gas enters a building	
 Which appliances run on electricity? Some appliances use batteries and some use mains electricity. Batteries come in different sizes depending on how much and for how long the appliance is used. Common appliances that use electricity. toaster lamp kettle Laptop X-box phone torch headlights television 	circuit	a complete route which an electric current can flow around	Motor	a device that uses electricity or fuel to produce movement	
	component	the parts that something is made of	Mains	where the supply of water, electricity , or gas enters a building	
	conductor	a substance that heat or electricity can pass through or along	Motor	a device that uses electricity or fuel to produce movement	
	current	a flow of electricity through a wire or circuit	Power	Power is energy, especially electricity, that is obtained in large quantities from a fuel source and used to operate lights, heating, and machinery	
	device	an object that has been invented for a particular purpose	source	where something comes from	
	Electricity	a form of energy that can be carried by wires and in used for heating and lighting, and to p rovide power for devices	Switch	a small control for an electrical devic which you use to turn the device on or off	
	motor	a device that uses electricity or fuel to produce movement	Switch	a small control for an electrical device which you use to turn the device on or off	
			Wires	a long thin piece of metal that i s used to fasten things or to carry electric current	



Knowledge is Power...

Ivington CofE Primary and Preschool



Reaching together... stand firm in your faith, be courageous and strong - 1 Corinthians 16:13

APPLIANCES

Many everyday appliances rely on electricity for them to work. Some appliances use mains electricity (are plugged into a socket) and others have a battery to make them work. Examples of mains-powered appliances include toasters and televisions. Battery-powered appliances can include mobile phones and torches.

HOW DOES A CIRCUIT WORK?

A complete circuit is a loop that allows electrical current to flow through wires.

- A circuit contains a battery (cell), wires and an appliance that requires electricity to work (such as a **bulb.** motor or **buzzer**).
- The **electrical current** flows through the wires from the battery (cell) to the bulb, motor or buzzer).
- A switch can break or reconnect a circuit.
- A **switch** controls the flow of the **electrical current** around the **circuit**. When the **switch** is off, the **current** cannot flow. This is not the same as an incomplete circuit.

WHAT ARE ELECTRICAL CONDUCTORS AND **INSULATORS?**

When objects are placed in the **circuits**, they may or may not allow **electricity** to pass through.

- Objects that are made from materials that allow electricity to pass through a create a complete circuit are called electrical conductors.
- Objects that are made from materials that donot allow electricity to pass through and do not complete a circuit are called electrical insulators.

COMPLETE CIRCUIT	INCOMPLETE CIRCUIT		
Electricity can flow. The components will	There is a break in the circuit that prevents the		
work.	Electricity from flowing. The components will not work.		
DIAGRAM - CIRCUIT	INVENTOR – THOMAS EDISON		
	Thomas Edison was born in 1847 and died in 1931. He lived in the state of New Jersey in the United States of America (USA) He is known as one of the greatest inventors in history. He invented the light bulb, the Phonograph (which could record and play sound) and an early video camera called the Kinetograph. The films were then watched on a Kinetoscope which he also invented.		
SWITCHES			

Switches can be used to close or open a circuit. When off, a switch 'breaks' the circuit to stop the flow of electricy. When on, a switch 'completes' the circuit and allows the electricity to flow around the circuit.



Toggle switch



push button switch